

Siemens S7-1200

CPU 1212C AC/DC/Relay

Bit Logic Operations

- SET and RESET Instructions
- **Exercise Example**



Code and Compile
Learning Made Easy



www.codeandcompile.com



Bit Logic Instructions in LAD – SET and RESET (1) </>

SET Instruction


Symbol

  

When **S (Set)** is **activated**, then the data value at the **OUT** address is **set to 1**. When **S** is **not activated**, OUT is **not changed**.


RESET Instruction

Symbol

 

When **R (Reset)** is **activated**, then the data value at the **OUT** address is **set to 0**. When **R** is **not activated**, OUT is **not changed**.

Example

 


Exercise Example in Ladder




Write a Logic to latch two outputs Q0.0 & Q0.1 with I0.0 and unlatch it using I0.1

Ladder Solution

 

PLC Wiring

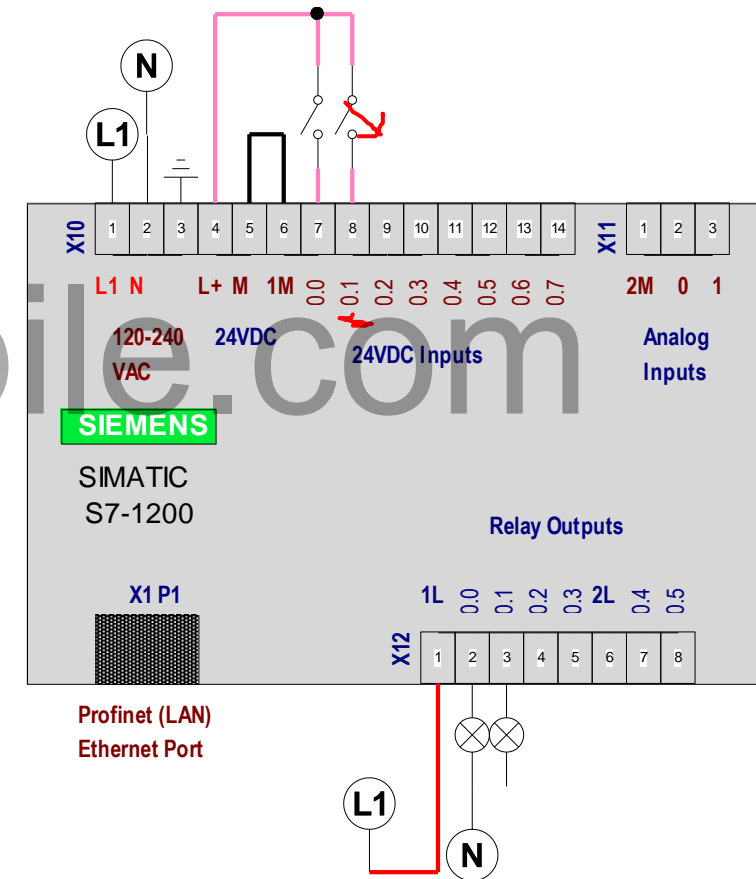

Required Condition


I0.0	I0.1	Q0.0	Q0.1
0	0	Last State	Last State
0	1	0	0
1	0	1	1
1	1	0	0

Bit Logic Instructions in FBD- SET & RESET (1)



SET Instruction


Symbol

 

When **S (Set)** is **activated**, then the data value at the **OUT** address is **set to 1**. When **S is not activated**, OUT is **not changed**.


RESET Instruction

Symbol

 

When **R (Reset)** is **activated**, then the data value at the **OUT** address is **set to 0**. When **R is not activated**, OUT is **not changed**.

Example

 


SET	RESET	OUT
I0.0	I0.1	Q0.0
0	0	Last State
0	1	0
1	0	1
1	1	0

Exercise Example in FBD



Write a Logic to latch two outputs Q0.0 & Q0.1 with I0.0 and unlatch it using I0.1


FBD Solution

 

Required Condition

I0.0	I0.1	Q0.0	Q0.1
0	0	Last State	Last State
0	1	0	0
1	0	1	1
1	1	0	0

PLC Wiring

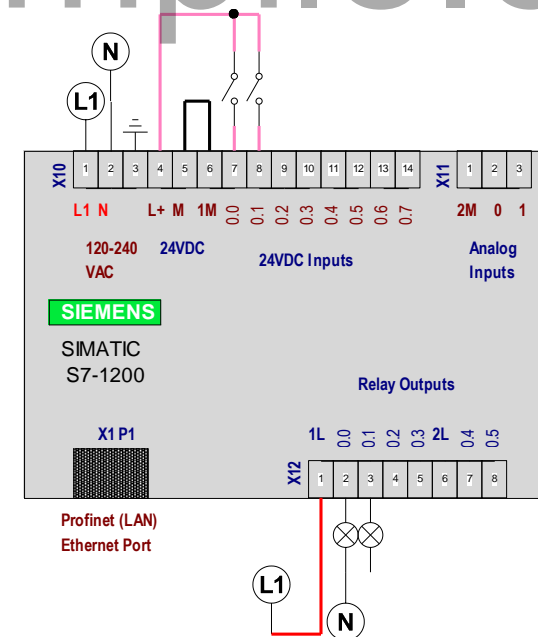


Bit Logic Instructions in LAD – SET and RESET (Field)




SET Instruction

Symbol

 

 When SET_BF is activated, a data value of 1 is assigned to "n" bits starting at address tag OUT. When SET_BF is not activated, OUT is not changed




RESET Instruction

Symbol



RESET_BF writes a data value of 0 to "n" bits starting at address tag OUT. When RESET_BF is not activated, OUT is not changed.

Example

 


SET	RESET	OUT 1	OUT 2	OUT 3
I0.0	I0.1	Q0.0	Q0.1	Q0.2
0	0	Last State	Last State	Last State
0	1	0	0	0
1	0	1	1	0
1	1	0	0	0

Exercise Example in LADDER



1. Write a Logic to latch three outputs Q0.0 ~ Q0.2 with I0.0 and unlatch all using I0.1


Ladder Solution

 

Required Condition

I0.0	I0.1	Q0.0	Q0.1	Q0.2
0	0	Last State	Last State	Last State
0	1	0	0	0
1	0	1	1	1
1	1	0	0	0


PLC Wiring

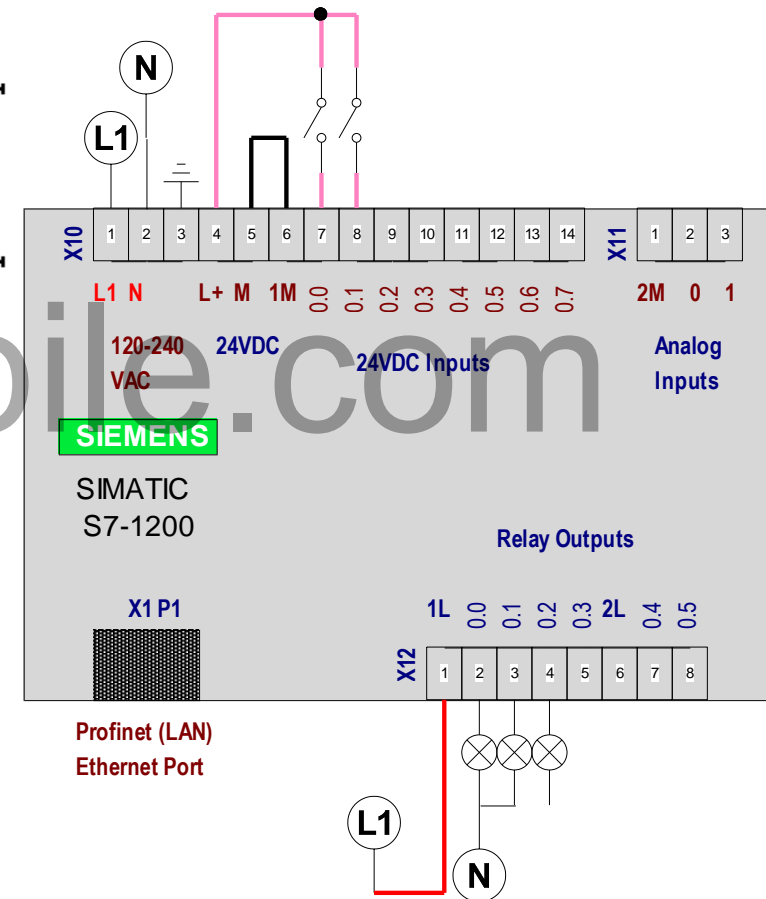

Bit Logic Instructions in FBD- SET & RESET (Field)

SET Instruction


Symbol

 

When SET_BF is activated, a data value of 1 is assigned to "n" bits starting at address tag OUT. When SET_BF is not activated, OUT is not changed


RESET Instruction

Symbol

 

RESET_BF writes a data value of 0 to "n" bits starting at address tag OUT. When RESET_BF is not activated, OUT is not changed.

Example

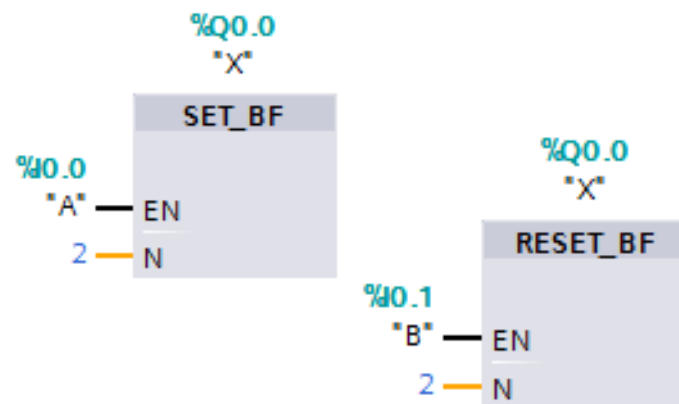

SET	RESET	OUT 1	OUT 2	OUT 3
I0.0	I0.1	Q0.0	Q0.1	Q0.2
0	0	Last State	Last State	Last State
0	1	0	0	0
1	0	1	1	0
1	1	0	0	0

Exercise Example in FBD

Write a Logic to latch three outputs Q0.0 ~ Q0.2 with I0.0 and unlatch all using I0.1

FBD Solution


Required Condition

PLC Wiring



SET/ Reset Flip Flop

Symbol

 


SR is a **reset dominant** latch where the **reset dominates**. If the **set (S)** and **reset (R1)** signals are both true, the value at address **Q0.0** will be 0.

Truth Table

SET	RESET	OUT 1
I0.0	I0.1	Q0.0
0	0	Last State
0	1	0
1	0	1
1	1	0

Reset/ SET Flip Flop

Symbol

 

RS is a **set dominant** latch where the **set dominates**. If the **set (S1)** and **reset (R)** signals are both true, the value at address **Q0.0** will be 1.

Truth Table

RESET	SET	OUT 1
I0.0	I0.1	Q0.0
0	0	Last State
0	1	1
1	0	0
1	1	0




Exercise Example in FBD



Write a Logic to latch the Motor Q0.0 with I0.0 (PB) and include two emergency switches I0.2 and I0.3 to unlatch it. Which Flip Flop you will use?

PLC Wiring

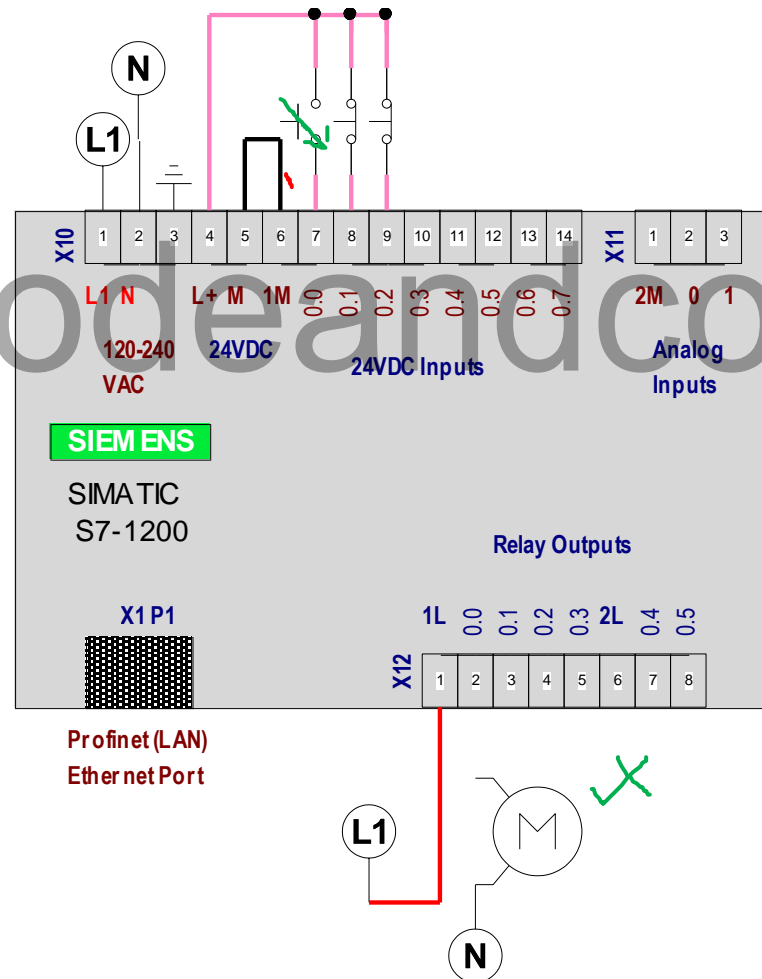


Required Condition

Contacts	Description
I0.0	Start the Motor
I0.2	Emergency Stop
I0.3	Emergency Stop
Q0.0	Motor

NP
1 0
1 0

FBD Solution

 

What did we learn in this lesson?

- The **SET & RESET Bit** instruction is used to latch or unlatch **only one bit**.
- The **SET & RESET Field instruction** is used to latch or unlatch **multiple bits**.
- In **SET/RESET Flip Flop** the OUTPUT will be **FALSE** if both the inputs are **HIGH**
- In **RESET/SET Flip Flop** the OUTPUT will be **TRUE** if both the inputs are **HIGH**

Thank you

*Get copy of this presentation
in the course!*



Code and Compile
Learning Made Easy

www.codeandcompile.com

