

Siemens S7-1200

CPU 1212C AC/DC/Relay

Bit Logic Operations

- Understanding NO/ NC and OUT
- **Exercise Example**



Code and Compile
Learning Made Easy

www.codeandcompile.com




Bit Logic Instructions in LAD - NO



Normally Open Contact

Symbol

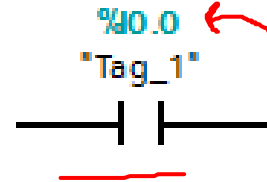


The Normally Open contact is **closed (ON)** when the assigned bit value **I0.0 is TRUE or equal to 1** and is **Open (OFF)** when **I0.0 is FALSE or equal to 0**.


Siemens TIA

Normally Open contact


Example in Series – AND Logic

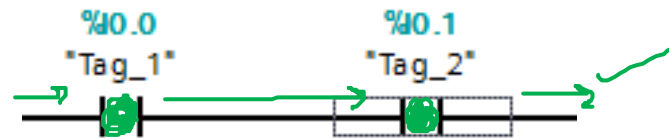

I0.0	I0.1	Output
0	0	FALSE
0	1	FALSE
1	0	FALSE
1	1	TRUE

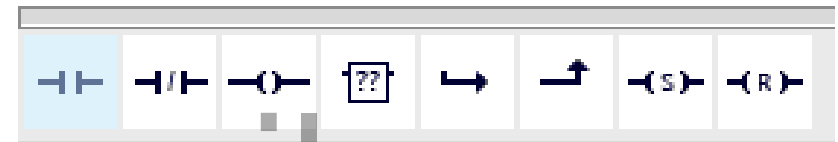

Example in Parallel- OR Logic

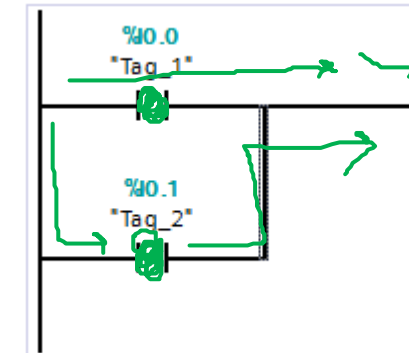


I0.0	I0.1	Output
0	0	FALSE
0	1	TRUE
1	0	TRUE
1	1	TRUE

Bit Logic Instructions in FBD- NO



Normally Open Contact

Symbol

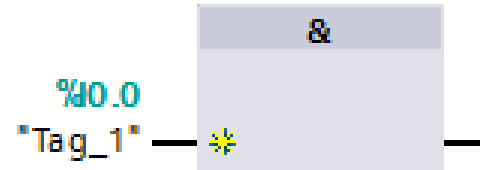


The block "&" is **TRUE** when the assigned bit value **I0.0** is **TRUE or equal to 1** and is **FALSE** when the assigned bit value **I0.0** is **FALSE or equal to 0**.

Siemens TIA

Normally Open contact




Example in Series – AND Logic

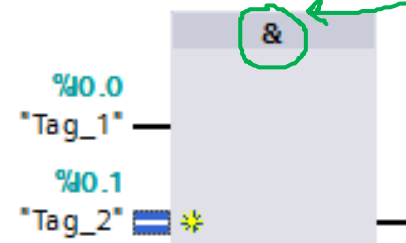

I0.0	I0.1	Output
0	0	FALSE
0	1	FALSE
1	0	FALSE
1	1	TRUE

Example in Parallel- OR Logic

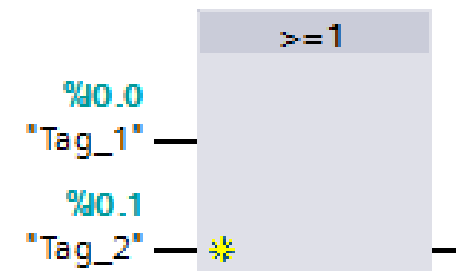

I0.0	I0.1	Output
0	0	FALSE
0	1	TRUE
1	0	TRUE
1	1	TRUE

Bit Logic Instructions in LAD- NC



Normally Close Contact

Symbol




%I0.0
"Tag_1"



The Normally Close contact is **closed (ON)** when the assigned bit value **I0.0** is **FALSE** or equal to 0 and it's **open (OFF)** when the assigned bit value **I0.0** is **TRUE** or equal to 1.

Siemens TIA

Normally Close contact

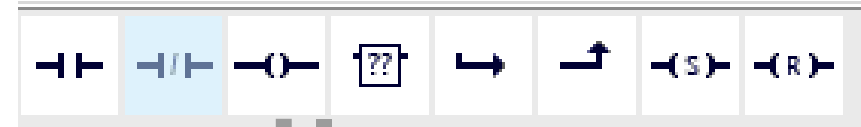


Example in Series – NOR Logic



I0.0	I0.1	Output
0	0	TRUE
0	1	FALSE
1	0	FALSE
1	1	FALSE

Example in Parallel- NAND Logic

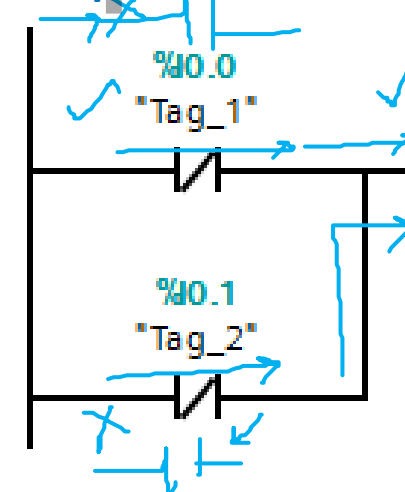


I0.0	I0.1	Output
0	0	TRUE
0	1	TRUE
1	0	TRUE
1	1	FALSE

Bit Logic Instructions in FBD- NC



Normally Close Contact

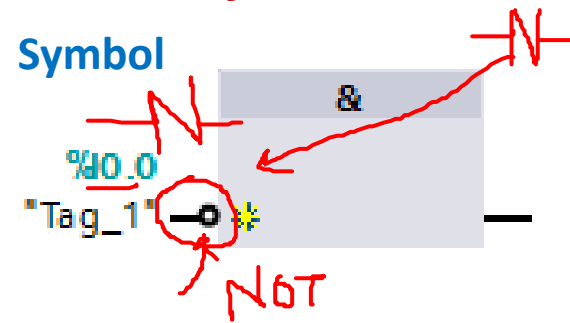


The block "&" is **TRUE** when the assigned bit value **I0.0** is **FALSE** or equal to 0 and is **FALSE** when the assigned bit value **I0.0** is **TRUE** or equal to 1

Siemens TIA

Normally close contact




Example in Series – NOR Logic

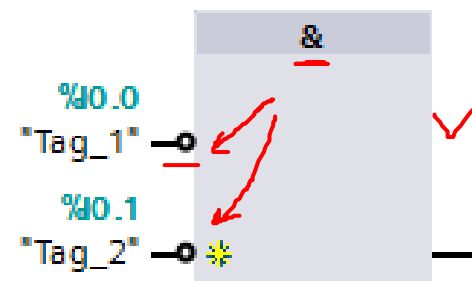

I0.0	I0.1	Output
0	0	TRUE
0	1	FALSE
1	0	FALSE
1	1	FALSE

Example in Parallel- NAND Logic

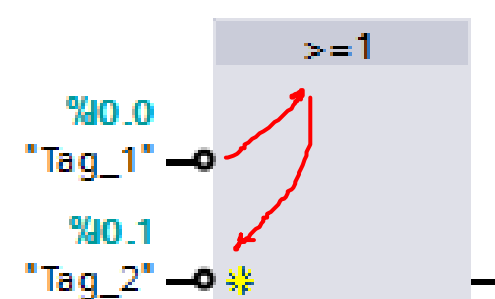

I0.0	I0.1	Output
0	0	TRUE
0	1	TRUE
1	0	TRUE
1	1	FALSE

Bit Logic Instructions in LAD & FBD- OUT




Output Coil

Ladder Symbol




FBD Symbol

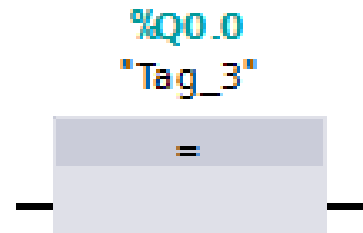


The **coil output instruction** writes a value for an output bit. The OUT instruction is **TRUE** when state before in the branch is **TRUE**

Siemens TIA

Output Coil

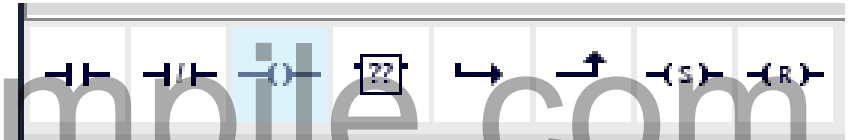

Example in Ladder

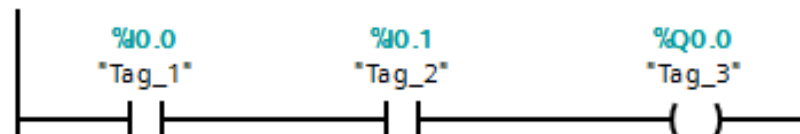

Example in FBD



Truth Table


I0.0	I0.1	Q0.0
0	0	FALSE
0	1	FALSE
1	0	FALSE
1	1	TRUE

Exercise Example





1. Design XOR gate such that output is TRUE if only one of the two inputs is TRUE. - Assume you have two toggle buttons connected to PLC input

Ladder Solution

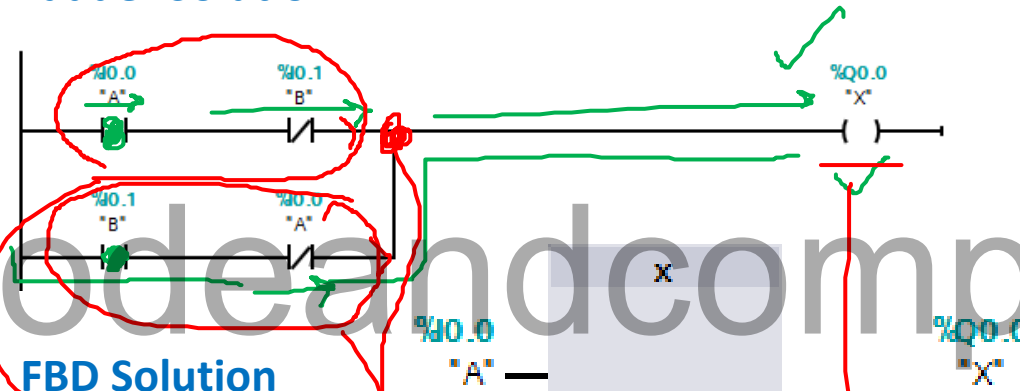

FBD Solution

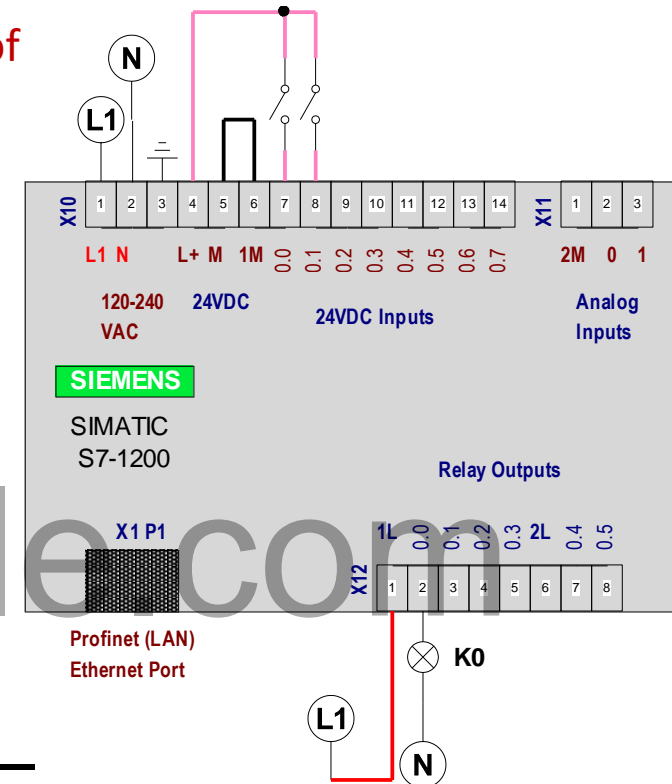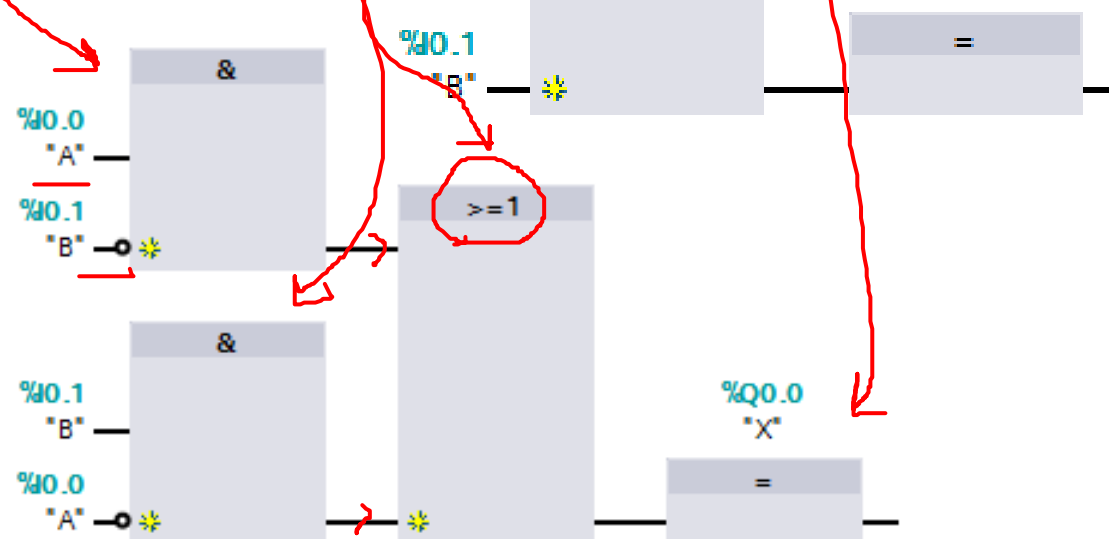

Required Condition

IO.0	IO.1	Q0.0
0	0	FALSE
0	1	TRUE
1	0	TRUE
1	1	FALSE

What did we learn in this lesson?

- The **Normally Open contact** is closed (**ON**) when the assigned bit value is **equal to 1**.
- The **Normally Closed contact** is closed (**ON**) when the assigned bit value is **equal to 0**.
- The LAD **NOT contact** **inverts** the logical state of power flow input.
- If there is power flow through an output coil or an FBD "**=**" box is **enabled**, then the **output bit** is **set to 1**.

Thank you

*Get copy of this presentation
in the course!*



Code and Compile
Learning Made Easy

www.codeandcompile.com

