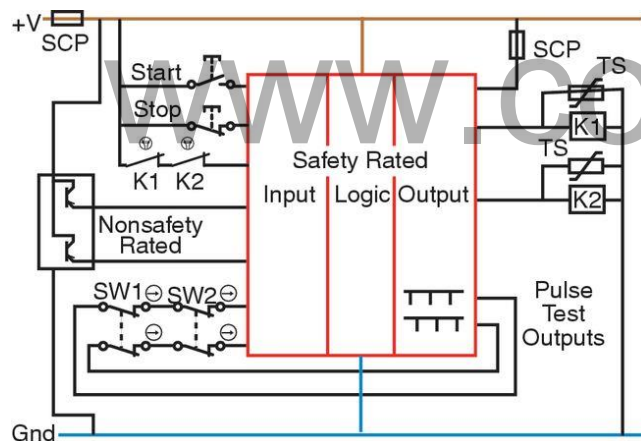


# Siemens S7-1200

CPU 1212C AC/DC/Relay

## PLC Safety Circuits

### PLC Safety Circuits via Fuse, Emergency Switches and Fault Protection Relays





**Code and Compile**  
Learning Made Easy

[www.codeandcompile.com](http://www.codeandcompile.com)




## PLC Power Requirement

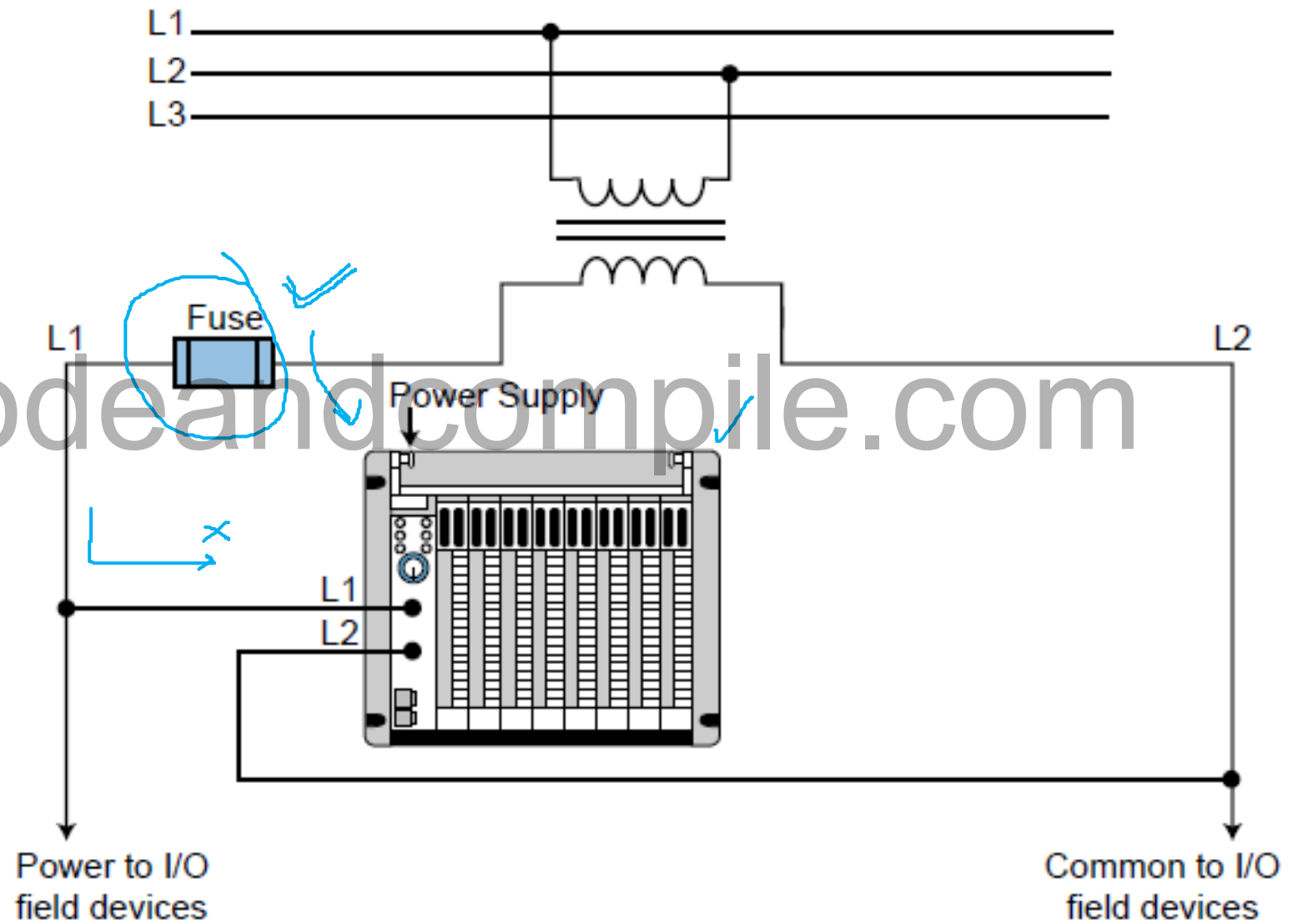

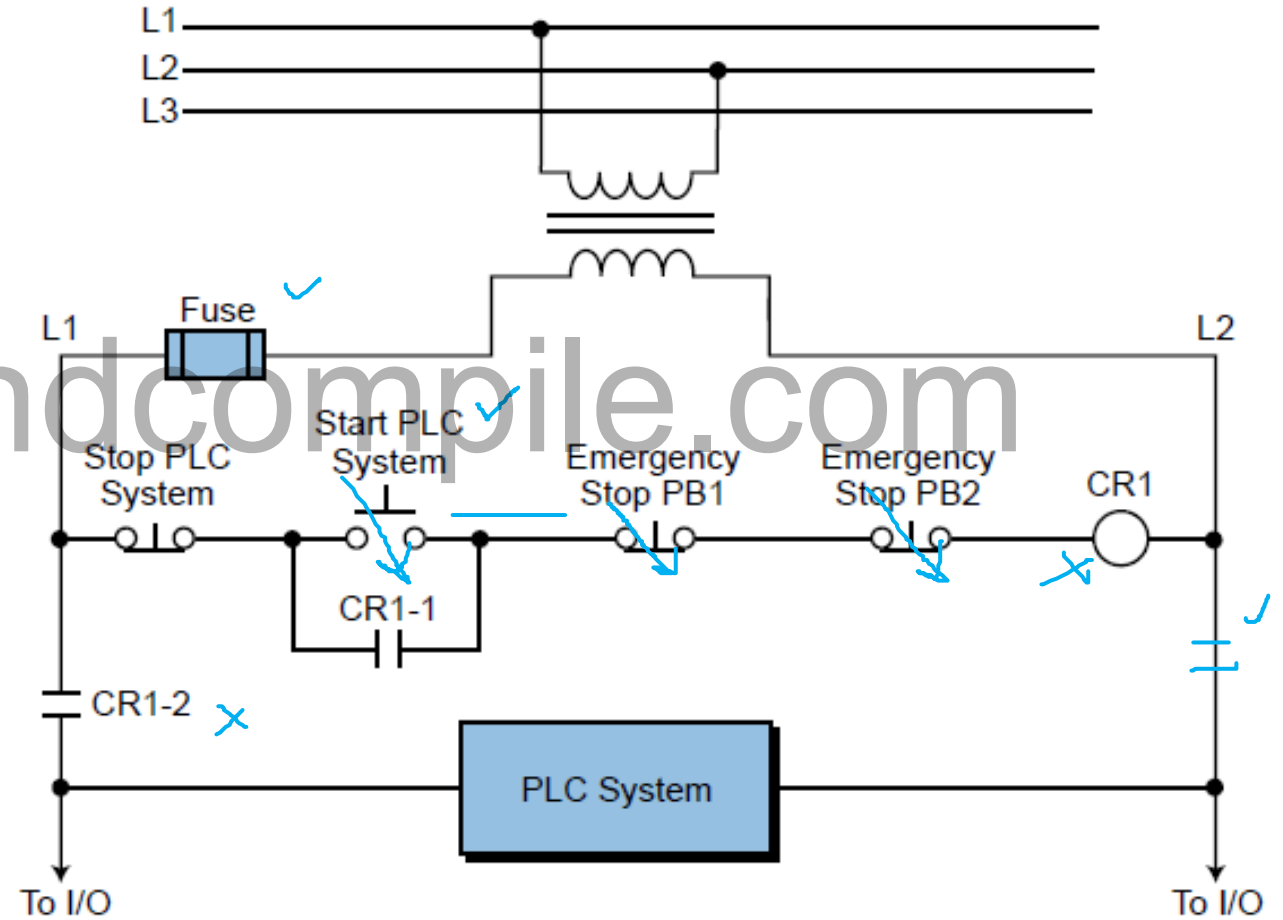
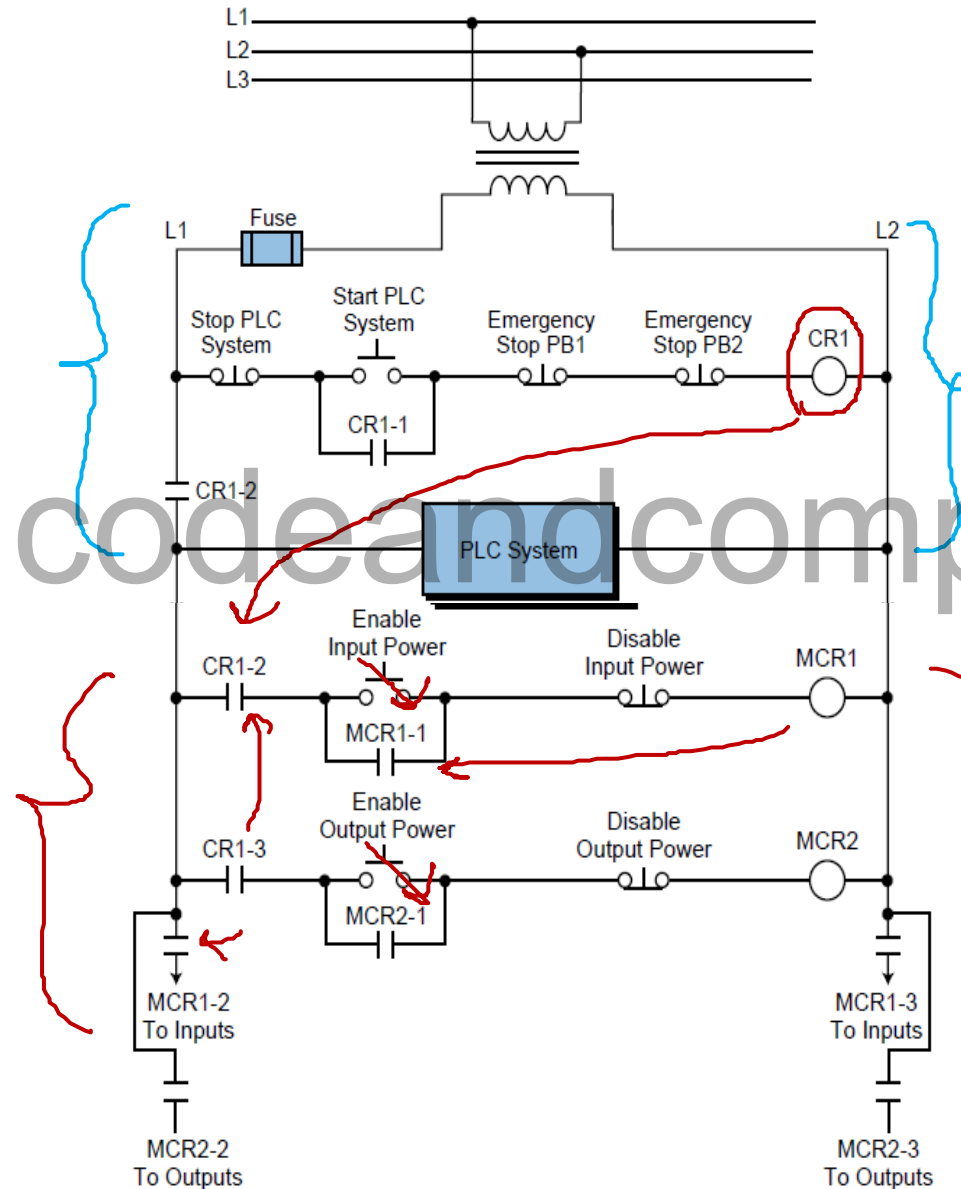
# PLC Safety Circuits –Master and Safety Control Relays





In this circuit we have used **Master control relays** to isolate the **input** and **output** power of PLC.

Thus we can **control the operation** of **Input** and **Output** of PLC's **independently** and can shut these down in case of **Emergency or Maintenance** without needing **to turn off the while PLC system**


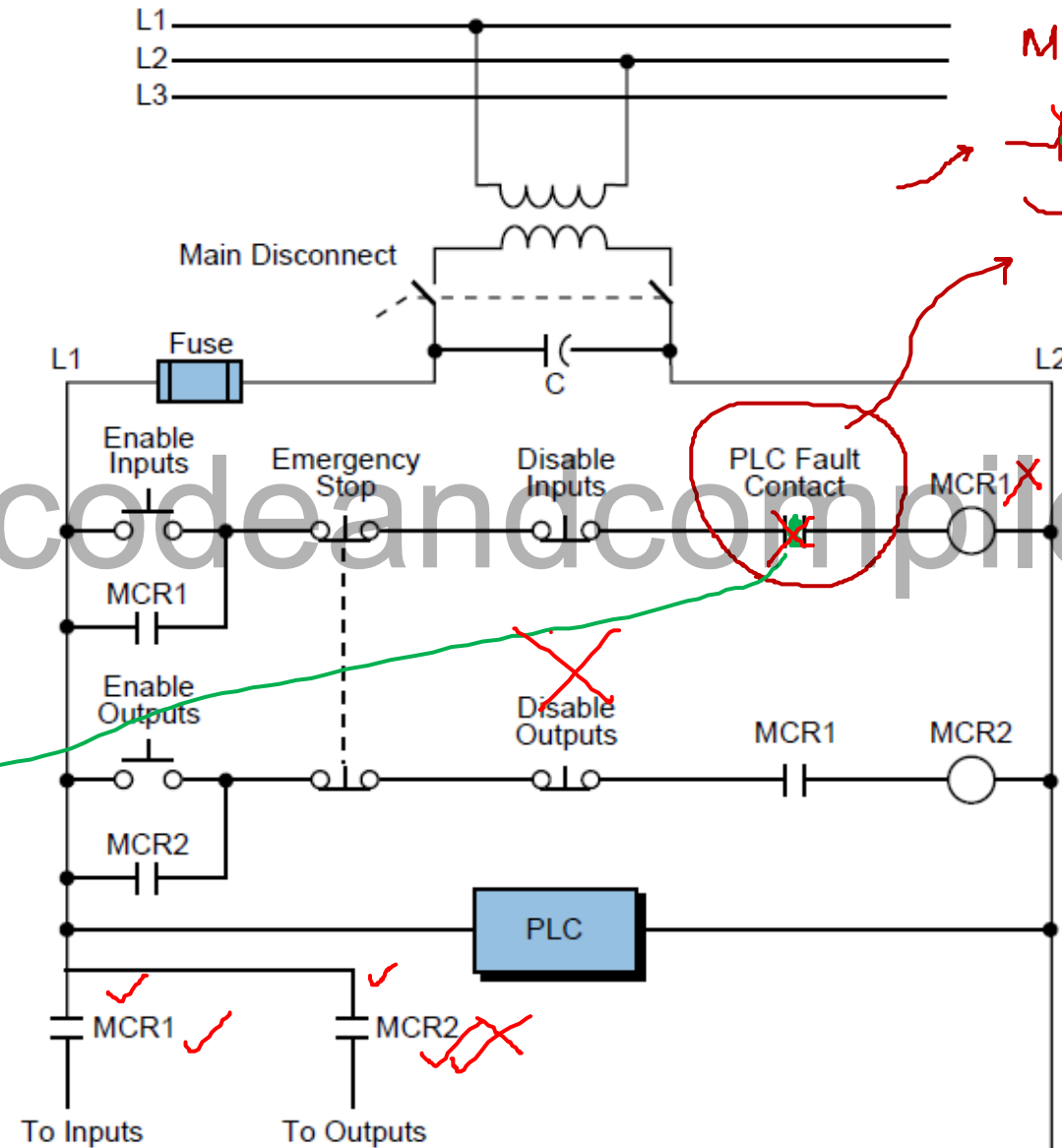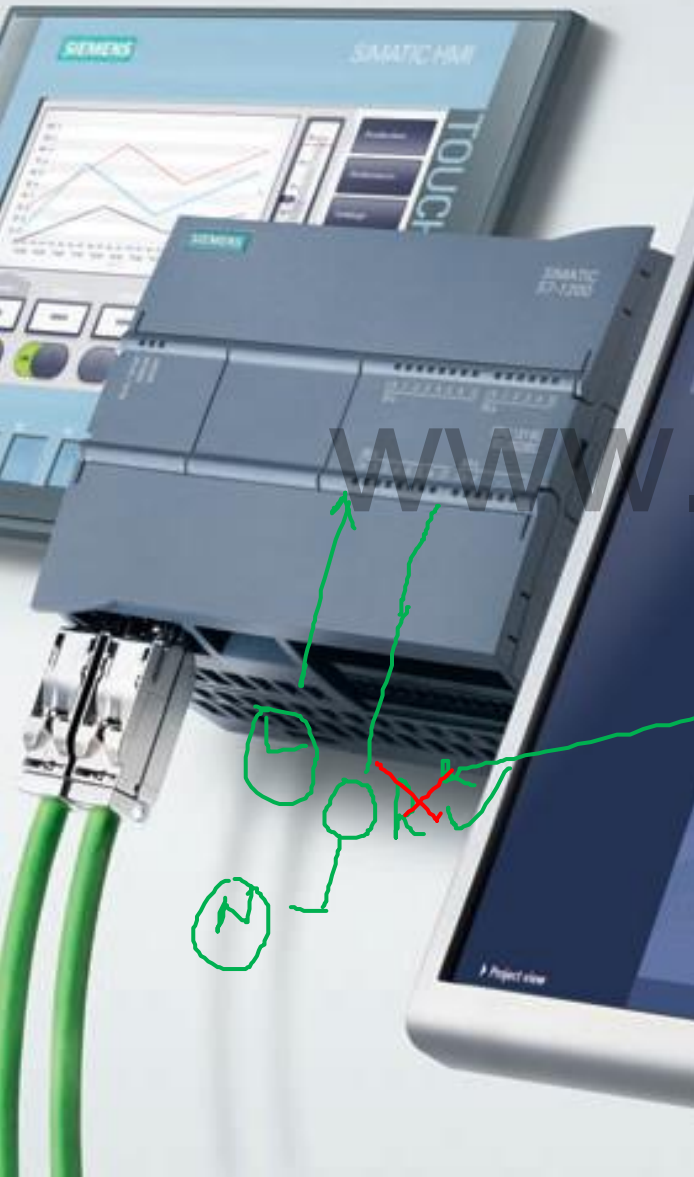
# PLC Safety Circuits - Fault Contact Protection



An MCR circuit may be extended by placing a **PLC fault relay** (closed during normal PLC operation) in series with any other **emergency stop condition**.

This enhancement will cause the MCR circuit to **cut the I/O power** in the case of a **PLC failure (memory error, I/O communications error, etc)**

## What did we learn in this lesson?

- To safeguard the PLC we can install **Fuse, Safety switches or relays** \_\_\_\_\_

Thank you

*Get copy of this presentation  
in the course!*



**Code and Compile**  
Learning Made Easy

[www.codeandcompile.com](http://www.codeandcompile.com)

