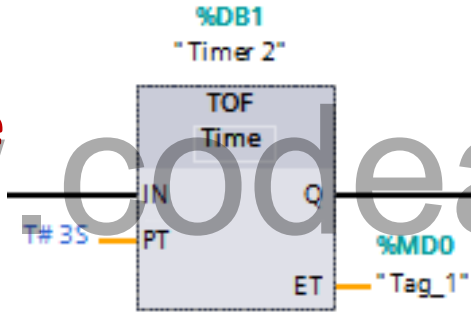


Siemens S7-1200

CPU 1212C AC/DC/Relay

Timer Operations (TOF)

- **Off-Delay**
- **Exercise Example**



Code and Compile

Learning Made Easy

www.codeandcompile.com


Timer Operations in LAD – TOF (OFF Delay Timer)




OFF Delay Timer

The **TOF** timer sets the output (Q) to **ON** and then **resets the output to OFF** after a **preset time delay**.

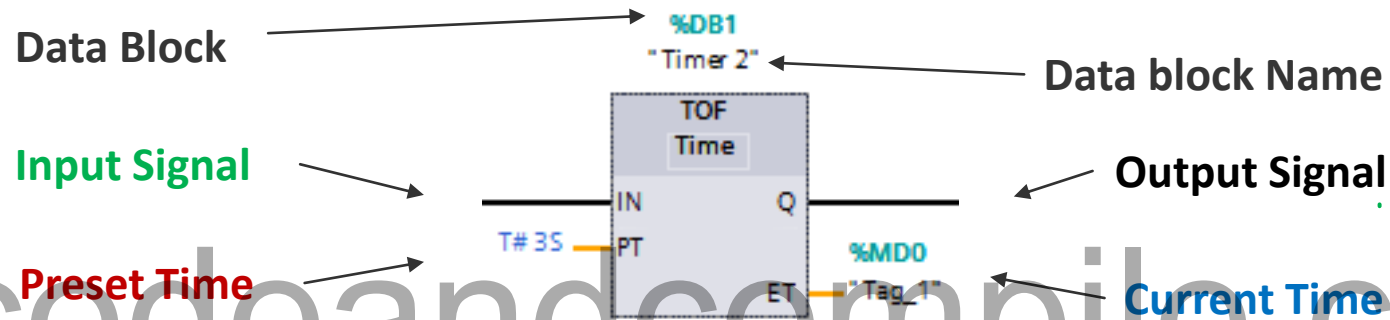Basic instructions
Name
Timer operations
TP
TON
TOF
TONR



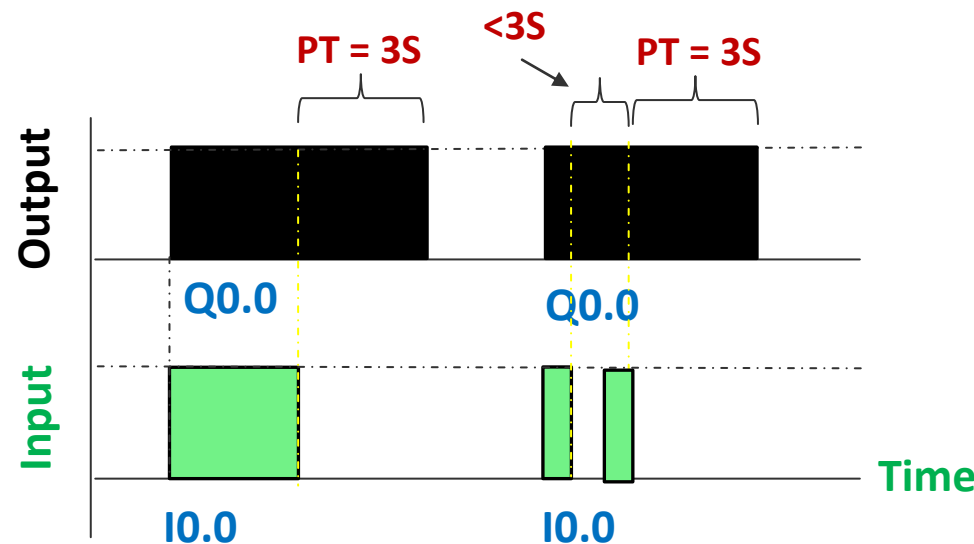Example If Preset Time is 3000ms = 3 second



DID YOU
KNOW



- Changing PT has **no effect** while the **timer runs**.
- Changing **IN** to **TRUE**, while the **timer runs**, **resets** and **stops** the timer.

init.




Exercise Example




Write a Logic to Latch the output Q0.0 for 5 seconds with momentary input signal I0.0


Ladder Solution

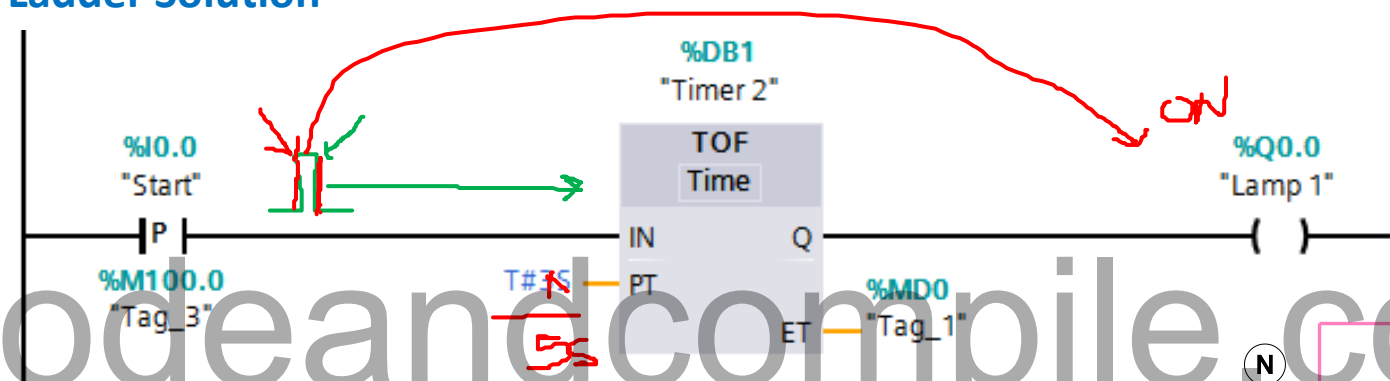

FBD Solution

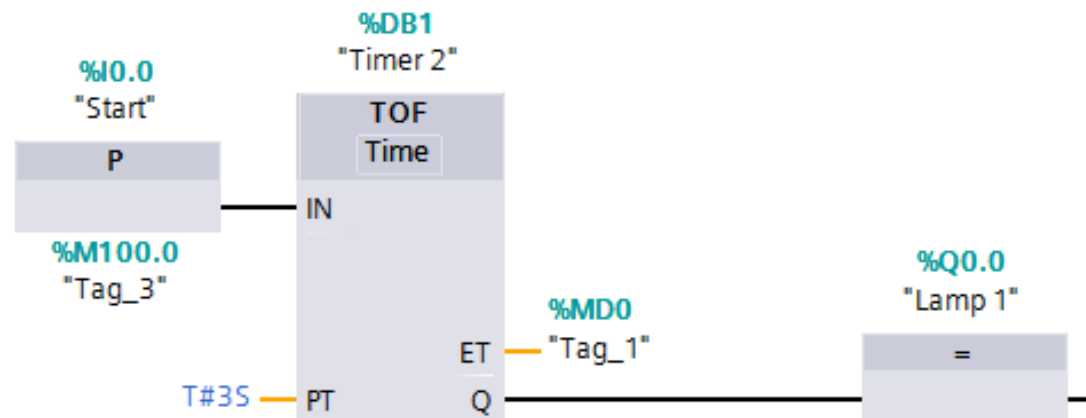

PLC Wiring

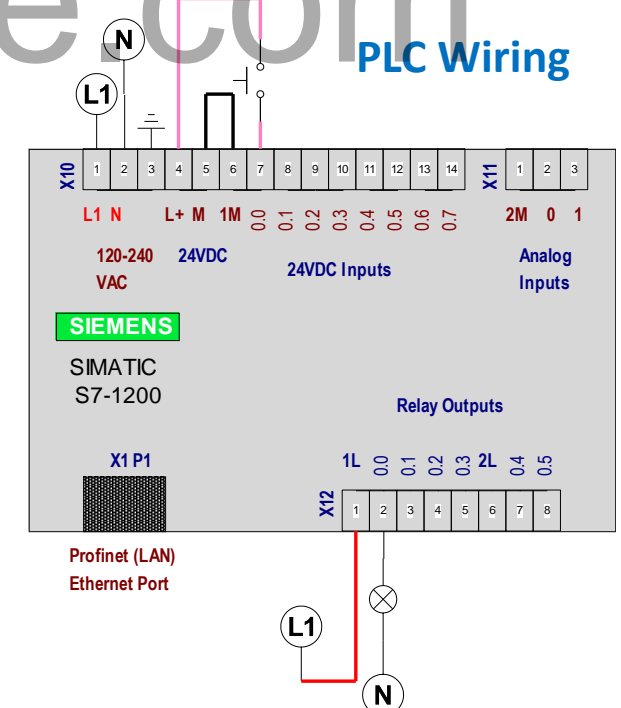


Exercise Example




Write a logic to achieve the following objective:

- Start a **Motor 1 (Q0.0)** with I0.0 (0 - 1) and after 10s delay start a **Motor 2 (Q0.1)**
- Stop the **Motor 1 (Q0.0)** with I0.0 (1 – 0) and after 10s delay stop the **Motor 2 (Q0.1)**

Ladder Solution

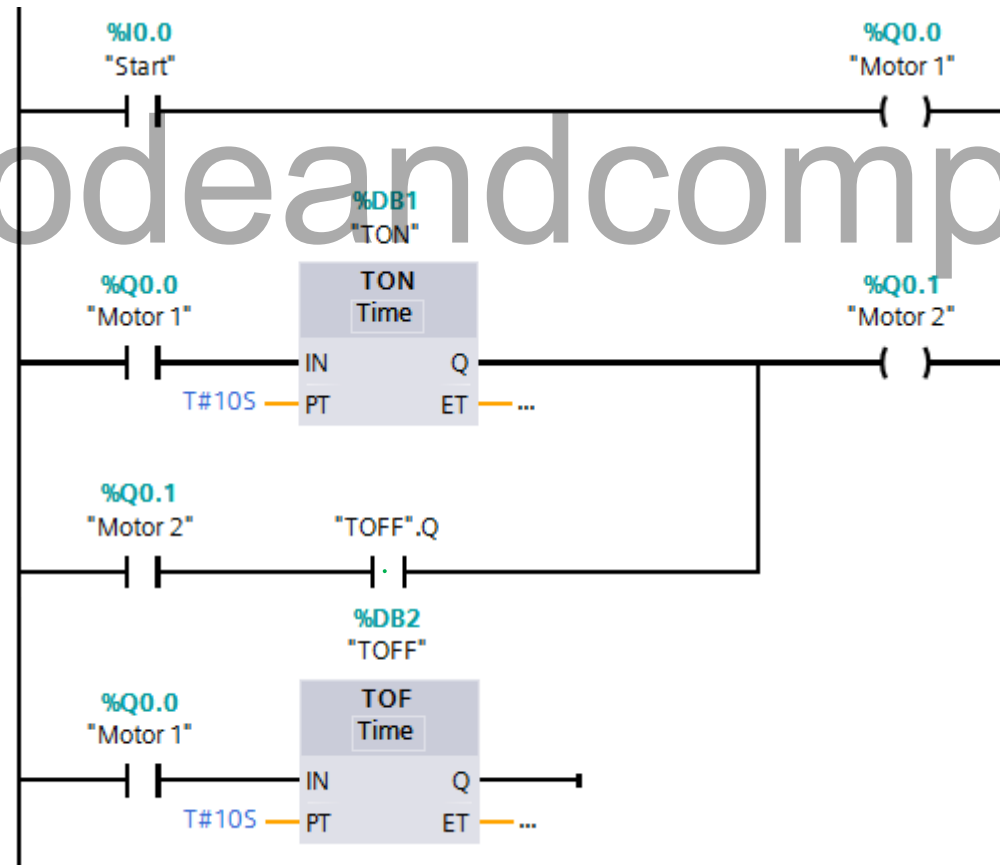

PLC Wiring

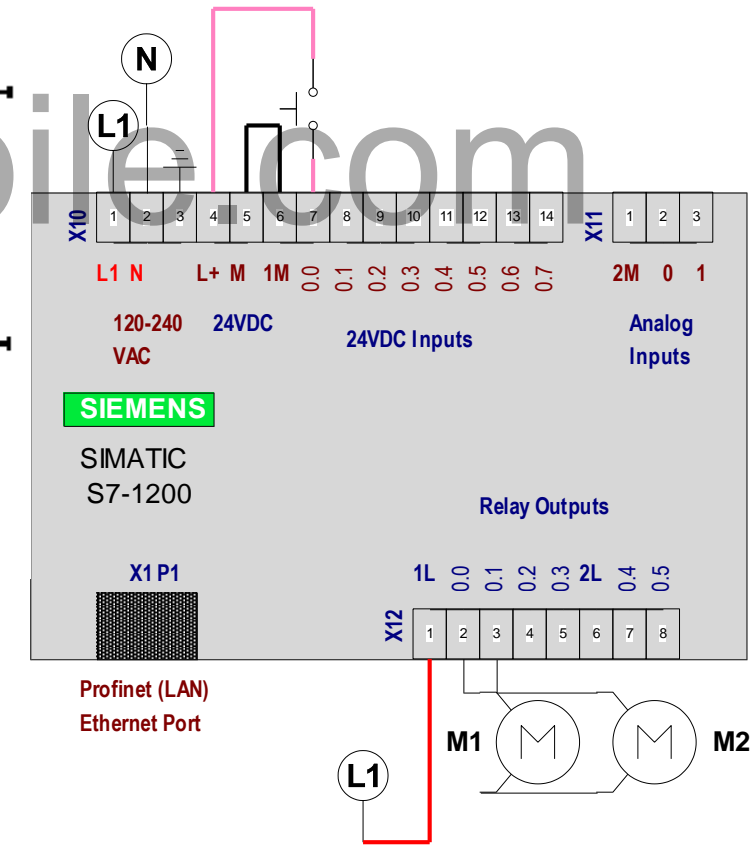



Exercise Example



Write a logic to achieve the following objective:

- Start a **Motor 1 (Q0.0)** with I0.0 (0 - 1) and after 10s delay start a **Motor 2 (Q0.1)**
- Stop the **Motor 1 (Q0.0)** with I0.0 (1 – 0) and after 10s delay stop the **Motor 2 (Q0.1)**

FBD Solution

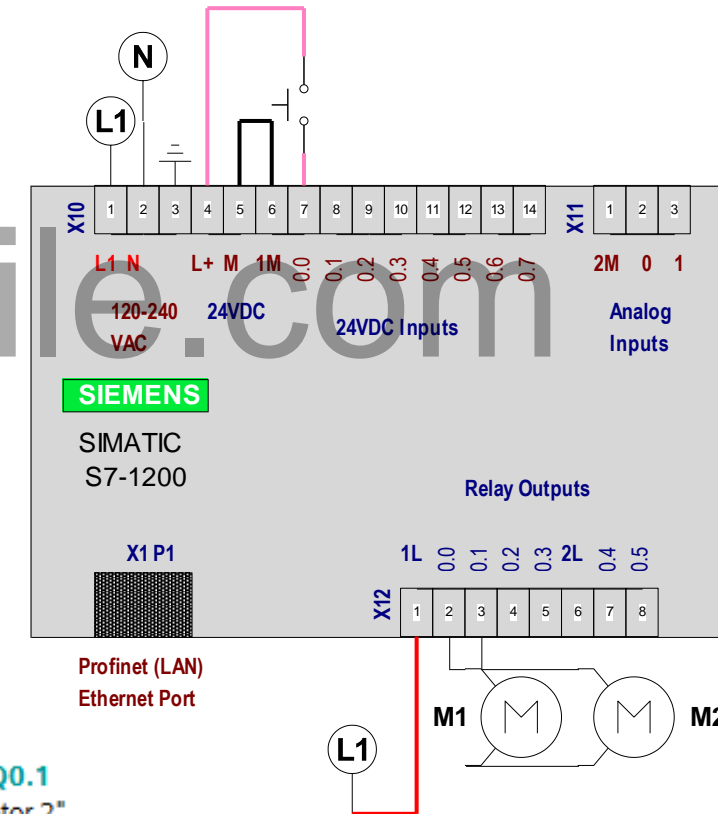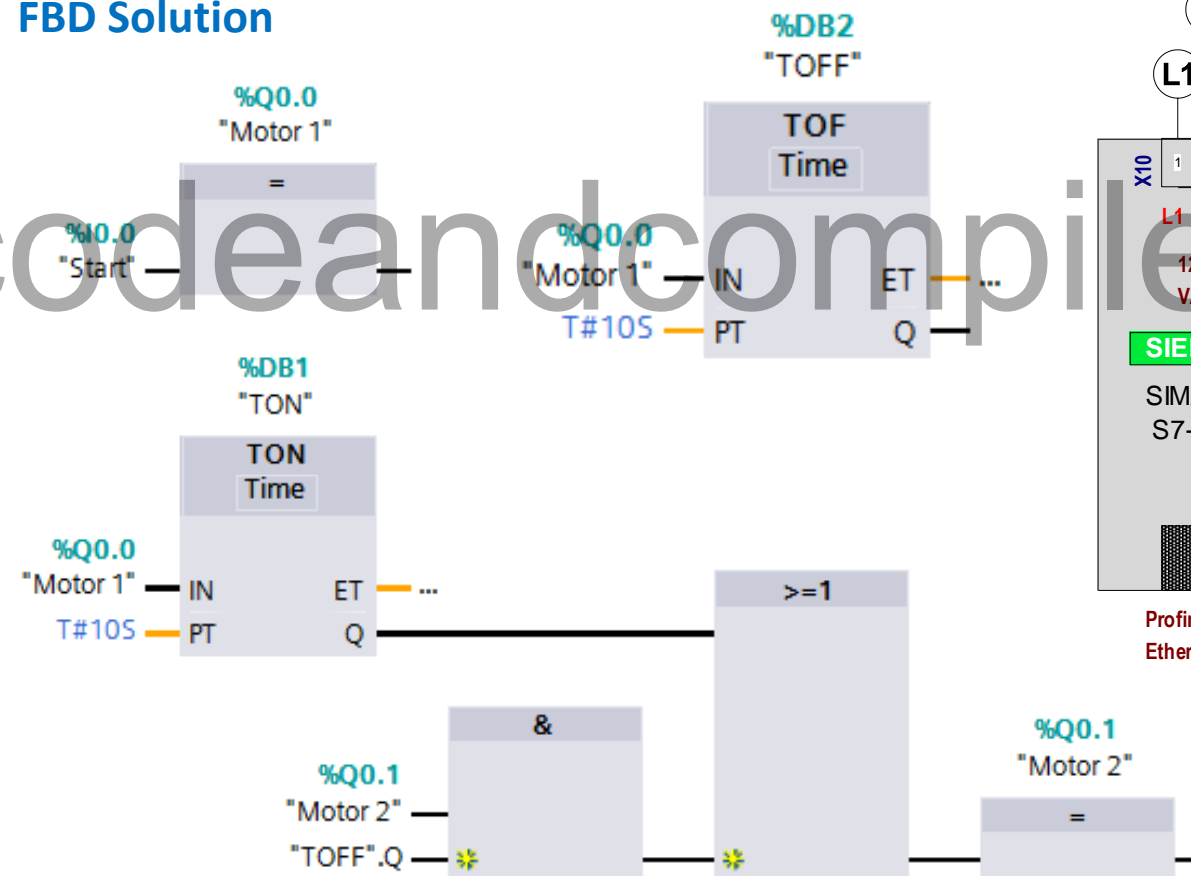

What did we learn in this lesson?

- **TOFF** is used to generate **OFF delay only**.
- The **parameters of TOFF** are stored in **Data block** which can be accessed anywhere in the logic by using the **specific address**.

Thank you

*Get copy of this presentation
in the course!*



Code and Compile
Learning Made Easy

www.codeandcompile.com

